

SHRIDEVI INSTITUTE OF ENGINEERING & TECHNOLOGY, TUMKUR-06
(An ISO 9001:2008 Certified Institution)
Department of Electrical & Electronics Engineering



Power System Analysis I(18EE62)
THIRD INTERNAL ASSESSMENT

Duration: 17 Minutes
date: 14.07.22

VI Semester
Max Marks: 40

NOTE: Answer two full questions

1.a) Derive an expression for the fault current when an LLG fault occurs on an unloaded generator through a fault impedance Z_f . Draw the inter connection of sequence networks. 10M(co-4)

b) A 400V star connected neutral grounded three phase generator is subjected to various types of faults. The fault currents for various types of faults are

i) Three phase --- 120 amperes

ii) L-L Fault --- 150 amperes


iii) L-G Fault --- 250 amperes

determine the sequence impedances. 10M(co-4)

2.a) Derive an expression for the fault current when an LL fault occurs on power system through a fault impedance Z_f . Draw the inter connection of sequence networks. 10M(co-4)

b) Derive an expression for the fault current when an LG fault occurs on an unloaded generator. Draw the inter connection of sequence networks. 10M(co-4)

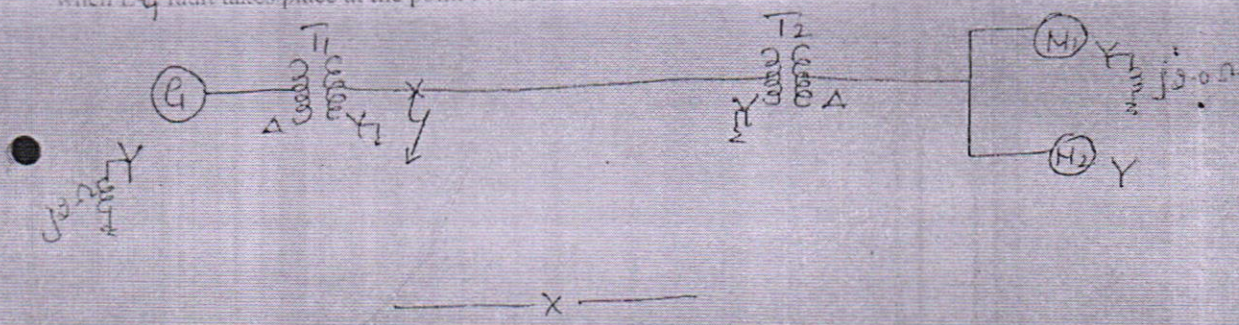3.a) A 30MVA, 13.8kV, 3 phase alternator has a $X_d=15\%$, $X_2=15\%$ & $X_0=5\%$ respectively. The alternator supplies two motors over a transmission line having transformers at both ends as shown in figure. The motors have rated inputs of 20MVA & 10MVA. Both 12.5kV with $X_d=20\%$, $X_2=20\%$ & $X_0=5\%$ respectively. Current limiting reactors of 2.0Ω each are in the neutral of the alternator and a large motor. The 3 phase transformers are both rated 35 MVA, 13.2 delta - 115 Y kV, with leakage reactance of 10%. Series reactance of the line is 80Ω . The zero sequence reactance of the line is 200Ω . Determine the fault current when L-G fault takes place at the point P. Assume $V_f=120kV$. 20M(co-4)



Handwritten signature

PRINCIPAL
SIET., TUMAKURU.

Power System Analysis - 1 (ISEE62)Scheme of Evaluation:1.a) Derivation: L-L-G fault.

Circuit diagram

Terminal conditions.

Symmetrical Component Relations

Interconnection of Sequence N/w

Sequence quantities

Expression for fault current.

→ 10M

$$\begin{array}{l}
 \text{b) } X_1 = 1.924 \Omega \\
 X_2 = 0.743 \Omega \\
 X_0 = 0.105 \Omega
 \end{array}
 \left. \vphantom{\begin{array}{l} X_1 \\ X_2 \\ X_0 \end{array}} \right\} \rightarrow 10M$$

2.a) Circuit diagram

Terminal conditions

Symmetrical component relations

Interconnection of Sequence N/w

Sequence quantities

Expression for fault current.

$$\begin{aligned}
 |I_f| &= \sqrt{3} I_{a1} \\
 &= \sqrt{3} \frac{E_a}{Z_1 + Z_2 + Z_0}
 \end{aligned}$$

→ 10M

b) L-L fault.

Circuit diagram

Terminal conditions

Symmetrical Component Relations.

Interconnection of Sequence N/w

Sequence quantities

Expression for fault current.


$$\begin{aligned}
 I_f &= 3 I_{a0} \\
 &= 3 \times \frac{E_a}{Z_1 + Z_2 + Z_0}
 \end{aligned}$$

→ 10M

3.a) Calculations of $(kV)_B$ values. → 2M


Calculations of Reactances (+ve, -ve & Zero Seq)

→ 4M

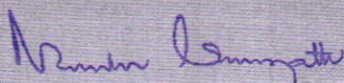


+ve Seq N/w

- Section
- No 19

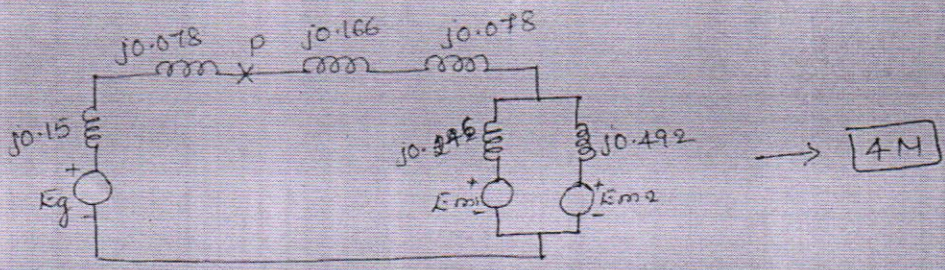


$Z_{1th} = j0.146 pu$

-ve Zero Seq N/w

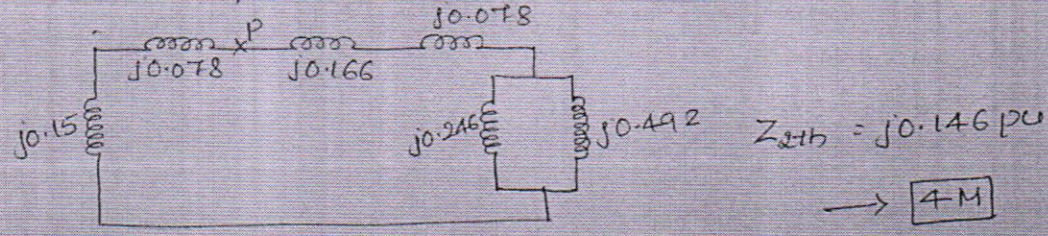

$Z_{2th} = j0.146 pu$

Zero Seq N/w

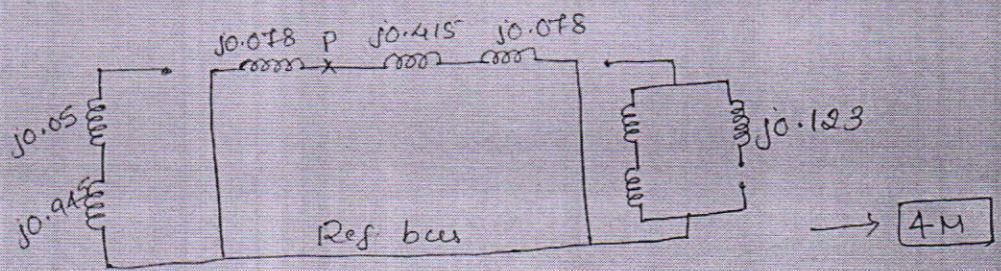

$Z_{0th} = j0.0673 pu$

LG fault $I_f = \frac{3V_{th}}{Z_{1th} + Z_{2th} + Z_{0th}} \rightarrow 2M$

$I_f = 8.339 pu$

Principals Signature

PRINCIPAL
SIET, TUMAKURU.